

# Notes for Physics 6B

## Circuit “Dividers”

### 0 Comment

You may find the formulae below useful, or you may just prefer to work from the fundamental equations every time you do a problem. The fundamental equations used to derive these formulae are the definition for resistance (Ohm’s law),  $V = \pm IR$ , the definition for capacitance,  $\pm Q = CV$ , Kirchhoff’s voltage law (or “loop rule”, to confirm that circuit elements in parallel have the same voltage), and Kirchhoff’s current law (or “junction rule”, to confirm the relationship between currents at a junction). Physical reasoning is also used to show that capacitors in series have the same polarity charges.

### 1 Resistors

- Voltage Dividers

Resistors in series “divide” the total voltage across them.

$$V_i = \frac{R_i}{R_{\text{eq}}} V$$

- Current Dividers

Resistors in parallel “divide” the total current through them.

$$I_i = \frac{R_{\text{eq}}}{R_i} I$$

### 2 Capacitors

- Voltage Dividers

Capacitors in series “divide” the total voltage across them.

$$V_i = \frac{C_{\text{eq}}}{C_i} V$$

- Charge Dividers

Capacitors in parallel “divide” the total polarity charge<sup>1</sup> on them.

$$Q_i = \frac{C_i}{C_{\text{eq}}} Q$$


### 3 Proofs

Here are some diagrams drawn to help you write your own proofs. Note that you should define the individual voltages  $V_i$  (where  $i = 1, 2, 3$ ) in the same direction as the total voltage  $V$ .

---


<sup>1</sup>Usually, capacitors have no net charge, since if one side has charge  $q$  the other side has charge  $-q$ . So I prefer to call  $q$  the “polarity charge” rather than “the charge on the capacitor”.

### Resistors in Series

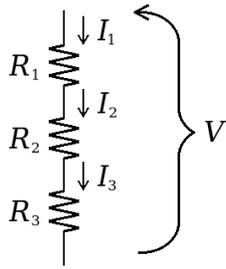


$$I_1 = I_2 = I_3 \equiv I$$
$$V = V_1 + V_2 + V_3$$

### Resistors in Parallel

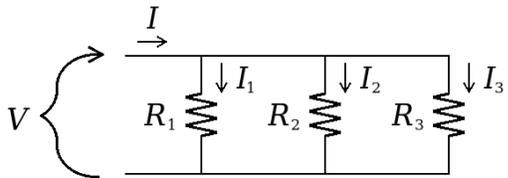


$$V_1 = V_2 = V_3 \equiv V$$
$$I = I_1 + I_2 + I_3$$

### Capacitors in Series

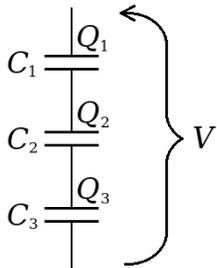

$$Q_1 = Q_2 = Q_3 \equiv Q$$
$$V = V_1 + V_2 + V_3$$

### Capacitors in Parallel

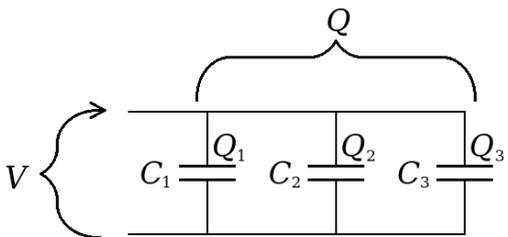

$$V_1 = V_2 = V_3 \equiv V$$
$$Q = Q_1 + Q_2 + Q_3$$